

2015级数电A.

王瑞 1120210446

1. $(53.5)_{10} = (65.4)_8 = (35.8)_{16}$

2. $(1010)_{10} = (1100)_{10} = \text{进判}$

3. 110000.01

4. $1111\ 1011$

5. $216 + 393 = 609 = 0110\ 0000\ 1001$

6. 1

7. $F = (A+B)(B+C)$

8. $0 F = \overline{C}D + \overline{A}B\overline{D}$

9. 20

10. $0.4V\ 0.5V$

11. $B\ 10\ \text{型}$

12. 上拉电阻

13. $R_S = 0$

14. Q_A

15. 4

~~15. 31, 16.~~

16. $31, 16$

17. 不考

18. 不考

19. 高电平, 低电平, 高电平

20. 5

21. 并行比较ADC

22. 10

2.

$$(1) F_1 = \pi M(4, 8, 9, 12, 13, 14) \\ = \sum m(4, 8, 9, 12, 13, 14)$$

$$F_2 = \pi M(0, 5, 10, 15) \\ = \sum m(0, 5, 10, 15)$$

$$F_3 = \pi M(1, 2, 3, 6, 7, 11) \\ = \sum m(1, 2, 3, 6, 7, 11)$$

(2) F_1, B, B_0

$A_1 A_0 \backslash B_1 B_0$	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	1	0	1
10	1	1	0	0

F_3, B, B_0

$A_1 A_0 \backslash B_1 B_0$	00	01	11	10
00	0	1	1	1
01	0	0	1	1
11	0	0	0	0
10	0	0	1	0

(3) $F_1 = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0$

(4) $F_3 = \bar{A}_1 B_1 + \bar{A}_0 B_1 B_0 + \bar{A}_1 \bar{A}_0 B_0$

	A_1	A_0	B_1	B_0	F_3	F_2	F_1
0	0	0	0	0	0	1	0
1	0	0	0	1	1	0	0
2	0	0	1	0	1	0	0
3	0	0	1	1	1	0	0
4	0	1	0	0	0	0	1
5	0	1	0	1	0	1	0
6	0	1	1	0	1	0	0
7	0	1	1	1	1	0	0
8	1	0	0	0	0	0	1
9	1	0	0	1	0	0	1
10	1	0	1	0	0	1	0
11	1	0	1	1	1	0	0
12	1	1	0	0	0	0	1
13	1	1	0	1	0	0	1
14	1	1	1	0	0	0	1
15	1	1	1	1	0	1	0

(5) F_1, F_2, F_3 : 比较 A, A_0 与 B, B_0 大小

B, B_0 大小

若 $A, A_0 > B, B_0$

则 $F_1 F_2 F_3 = 100$

若 $A, A_0 = B, B_0$

则 $F_1 F_2 F_3 = 010$

若 $A, A_0 < B, B_0$

则 $F_1 F_2 F_3 = 001$

11)

	A	B	C	X	Y
0	0	0	0	0	0
1	0	0	1	1	1
2	0	1	0	1	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	0	0
6	1	1	0	0	0
7	1	1	1	1	1

$$\frac{25}{9} = 2 \frac{7}{9}$$

(12) $X = \sum m(1, 2, 3, 7)$

$Y = \sum m(1, 2, 4, 7)$

X

BC	00	01	11	10
A=0	0	1	1	1
A=1	0	0	1	0


Y

BC	00	01	11	10
A=0	0	1	0	1
A=1	1	0	1	0


(13) $X = B(C + \bar{A}C + \bar{A}B)$
 $= B(C + \bar{A}C + \bar{A}B)$
 $= \bar{B}C \cdot \bar{A}C \cdot \bar{A}B$

$Y = A\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C + \bar{A}B\bar{C}$
 $= A \oplus B \oplus C$

(13) X

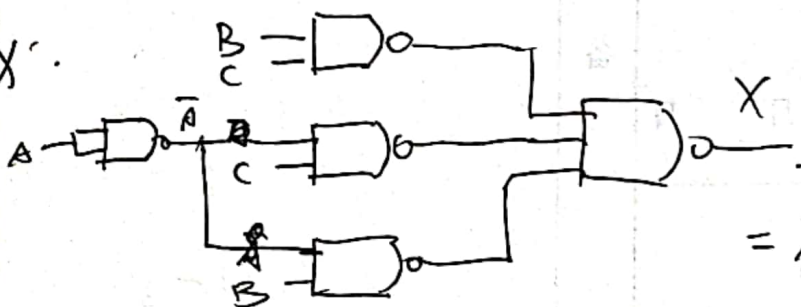

(14)

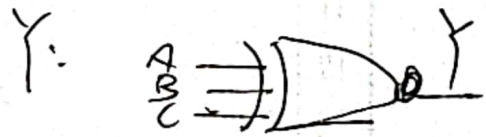

$= \bar{A}\bar{C} \cdot B + A\bar{C} \cdot 0 + \bar{A}C + AC \cdot B$
 $= m_0 \cdot B + m_2 \cdot 0 + m_1 + m_3 \cdot B$

(15) $X = B(C + \bar{A}C + \bar{A}B)$


$= \sum m(1, 2, 3, 7)$

$= \bar{A}\bar{B}(C + \bar{A}B\bar{C} + \bar{A}B\bar{C} + \bar{A}B\bar{C})$
 $= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{A}\bar{C} \cdot B + \bar{A}\bar{B}C \cdot B$

B	D ₃	
0	D ₂	
1	D ₁	
B	D ₀	S ₁ S ₀
		A C

3

④. (1) 原始状态图:

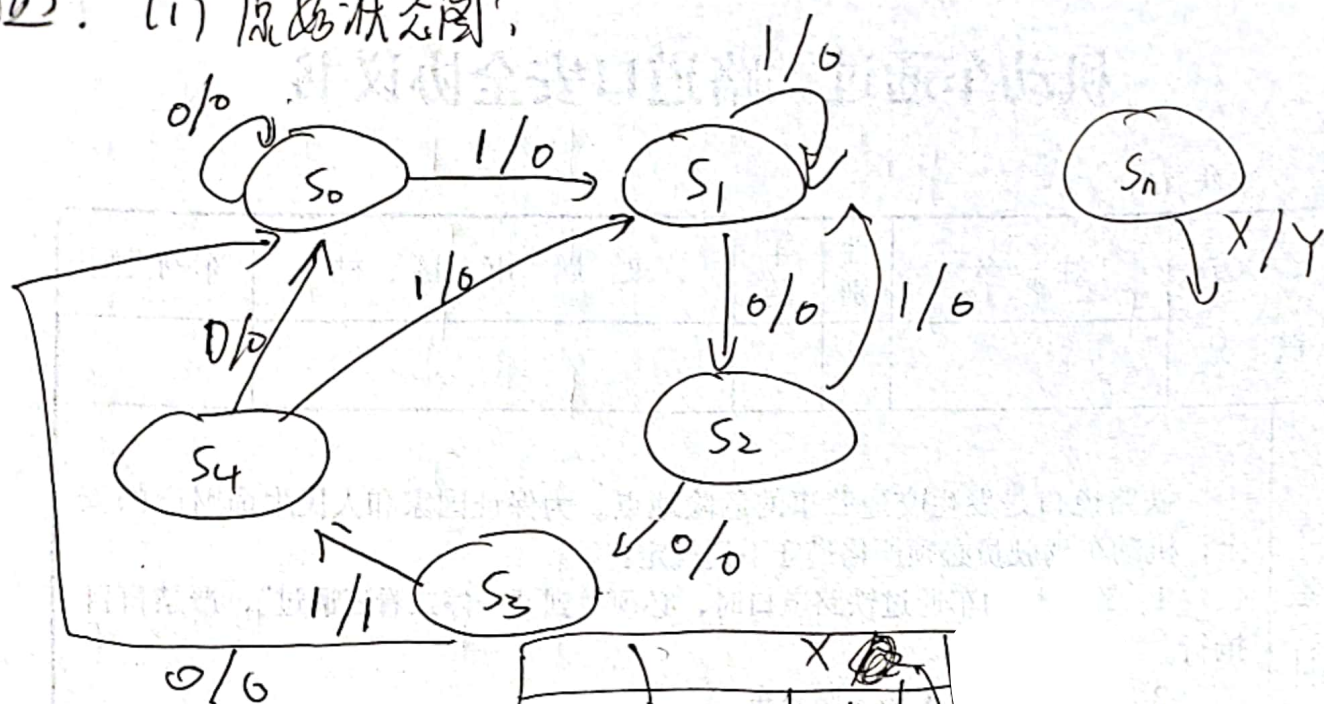


状态转换表

状态	0	1
S_0	$S_0/0$	$S_1/0$
S_1	$S_2/0$	$S_1/0$
S_2	$S_3/0$	$S_1/0$
S_3	$S_0/0$	$S_4/1$
S_4	$S_0/0$	$S_1/0$

由表可知, S_0, S_4 是等价状态



S_{n+1}/Y

故最简状态图为

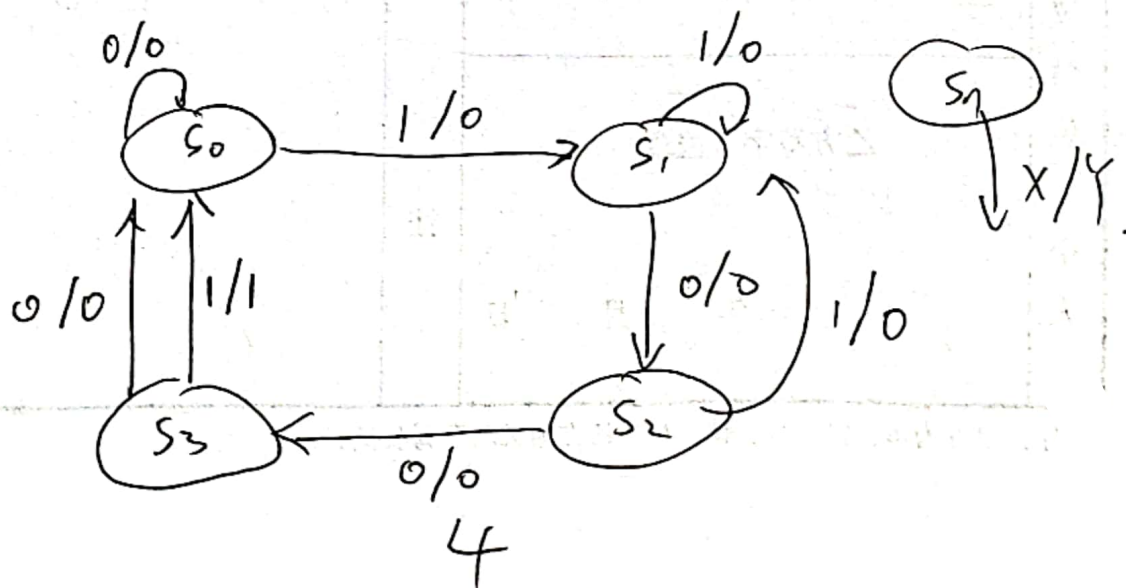

五. (1) 该电路具有移位功能, 且 Q_0 与 S_1 相连,
 当 Q_0 为 0 时正常右移, Q_0 为 1 时置位,
 故从置位状态开始, 每一个时钟一个
 时钟进行右移, 直到 $Q_0 = 1$ 置位.

故状态图如下所示:

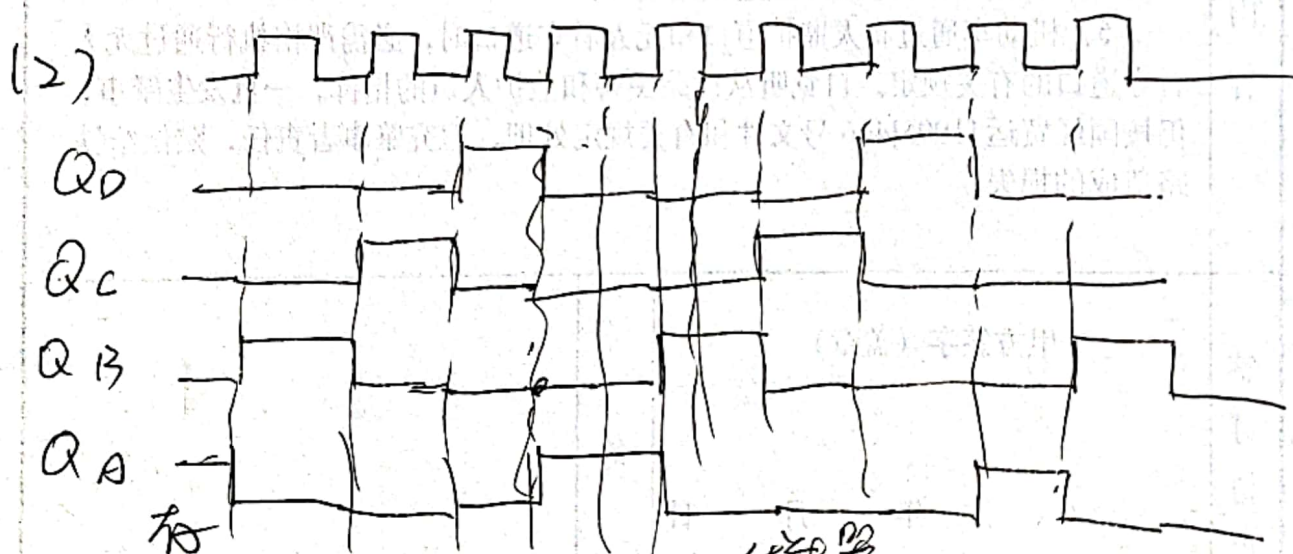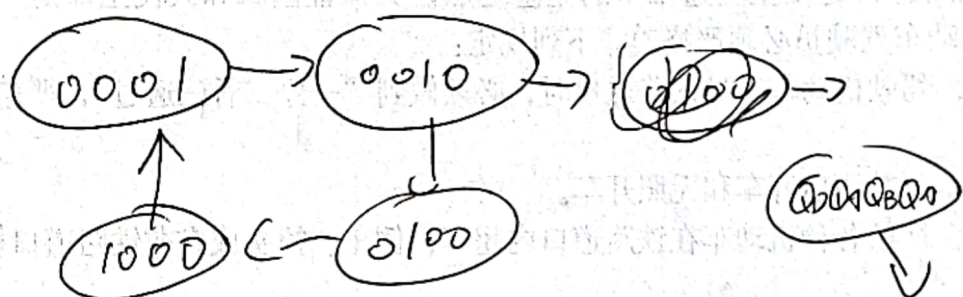


(3) 移位寄存器. 顺序脉冲发生器, $M=4$.
 也可作 0001 波形产生器


(4) 不能自启动, 全零状态无法在有限个周期
 如进入主循环.

0000 - 一直是 0000, 不能自启动.

六. (1) 根据题意, 可绘出如下状态转换图:

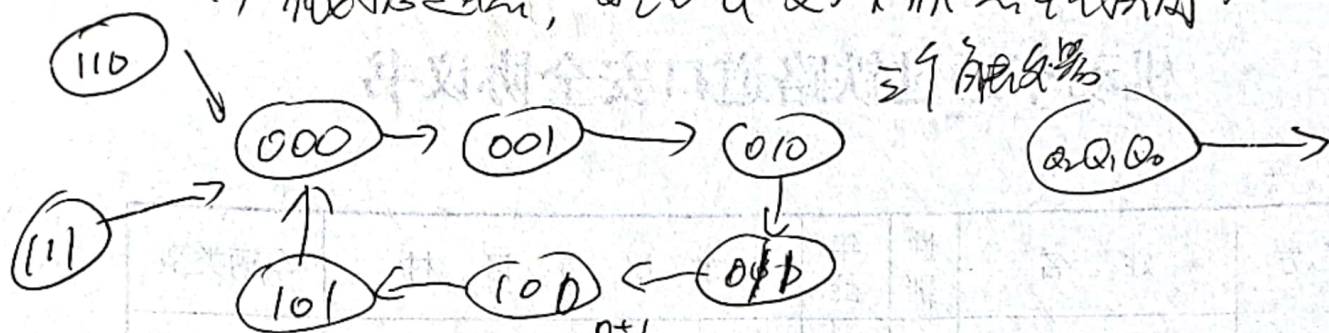

再绘出卡诺图为

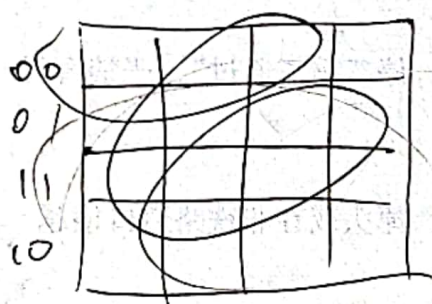

$$Q_2^{n+1}$$

Q_2	Q_1	Q_0	00	01	11	10
0	0	0	1	0		
1	1	0	0	0		

$$Q_2^{n+1} = \overline{Q_2} \overline{Q_1} \overline{Q_0} + \overline{Q_2} Q_1 \overline{Q_0}$$

$$Q_1^{n+1}$$

Q_1	Q_2	Q_0	00	01	11	10
0	0	1	0	1		
1	0	0	0	0		

$$Q_1^{n+1} = \overline{Q_2} \overline{Q_1} \overline{Q_0} + \overline{Q_2} Q_1 \overline{Q_0}$$

$$Q_0^{n+1}$$

Q_0	Q_2	Q_1	00	01	11	10
0	1	0	0	1		
1	1	0	0	0		

$$Q_0^{n+1} = \overline{Q_2} \overline{Q_1} \overline{Q_0} + \overline{Q_2} Q_1 \overline{Q_0}$$

$$Q_2^{n+1}$$

Q_2	Q_1	Q_0	00	01	11	10
0	1	0	1	0		
1	1	0	0	0		

$$J_2 = Q_1 Q_0$$

$$K_2 = \overline{Q_1} \overline{Q_0} \quad K_2 = Q_1 + Q_0$$

$$Q_1^{n+1}$$

Q_1	Q_2	Q_0	00	01	11	10
0	0	1	0	1		
1	0	0	0	0		

$$J_1 = \overline{Q_2} \overline{Q_0}$$

$$K_1 = \overline{Q_2} \overline{Q_0}$$

$$K_1 = Q_2 + Q_0$$


$$Q_0^{n+1}$$

Q_0	Q_2	Q_1	00	01	11	10
0	1	0	0	1		
1	1	0	0	0		


$$J_0 = \overline{Q_1} + \overline{Q_2} \quad J_0 = \overline{Q_1} + \overline{Q_2}$$

$$K_0 = 0 \quad K_0 = 1$$

(2) 完整状态转换图

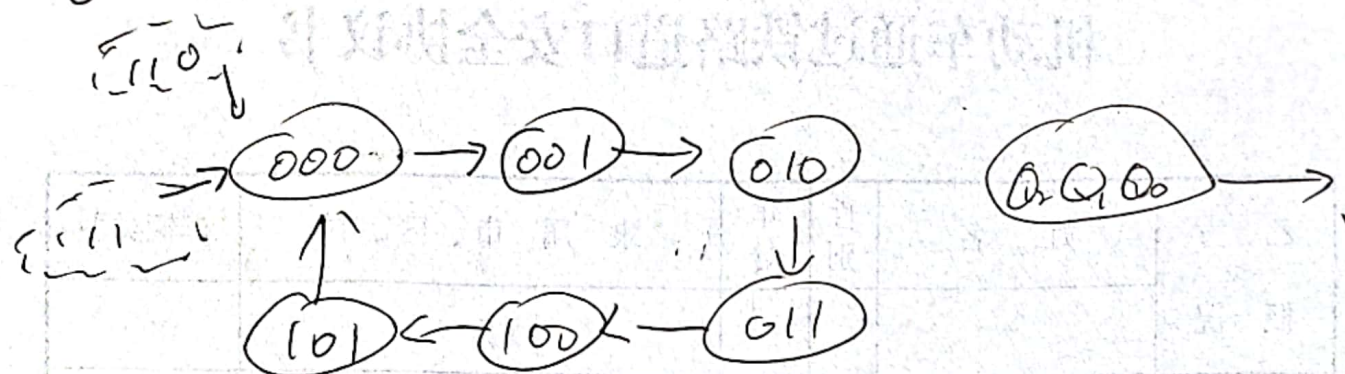

(3) 波形图

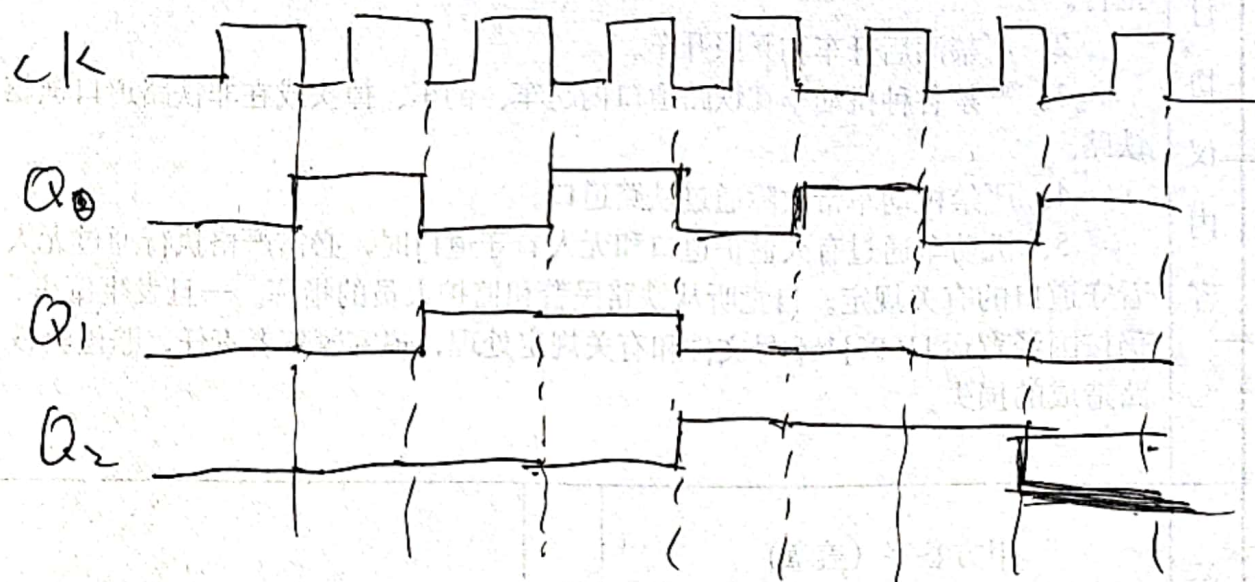

000 001 010 011 100 101

Q_0 二分频