

数电 2014级 期末

王翔

1120210446

一、(1) 3CA.B

(2) 155.5625

(3) 0100 0011 1000 . 1000

(4) 11001

(5) 11011011

(6) 4

(7) 最高位


(8) 输出只与当前状态机内部状态有关，而与输入无关

(9) 0, 2, 4, 5, 9, 10, 12, 15

(10) 一定

二、1.

(1)

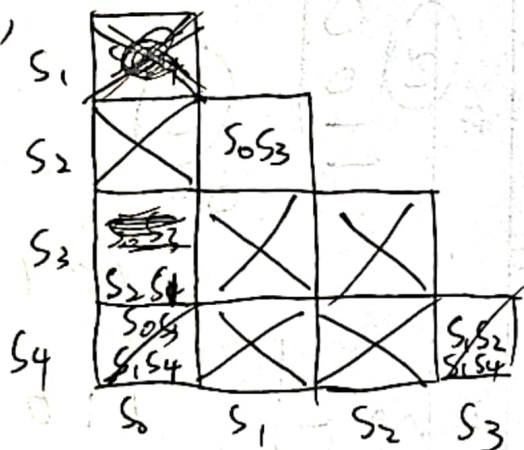

(2) S_0 与 S_3 等价

S_1 与 S_2 等价

理由：由隐含表可知

S_0 与 S_3 等价取决于 S_1 与 S_2 是否等价
而 S_1 与 S_2 是否等价取决于 S_0 与 S_3 是否等价
故 S_0 与 S_3 , S_1 与 S_2 等价

(3)

	00	01	1X
S_0	$S_0/1$	$S_1/0$	$S_4/1$
S_1	$S_0/0$	$S_4/0$	$S_1/1$
S_4	$S_0/1$	$S_1/0$	$S_1/1$


2. $Y = A\bar{C} + \bar{A}B + \bar{A}C$

当 $B=1$ $C=0$ 时, $Y = A + \bar{A}$

故 ~~C~~ 存在竞争条件.

由于 $Y = A + \bar{A}$, 故存在 ~~静态冒险~~ 静态 1 型冒险.

3.

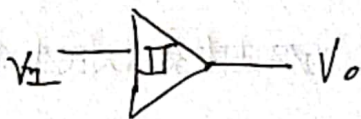


$V_T^+ = 2.2V$

$V_T^- = 1.4V$

$\Delta V = 0.8V$

4.

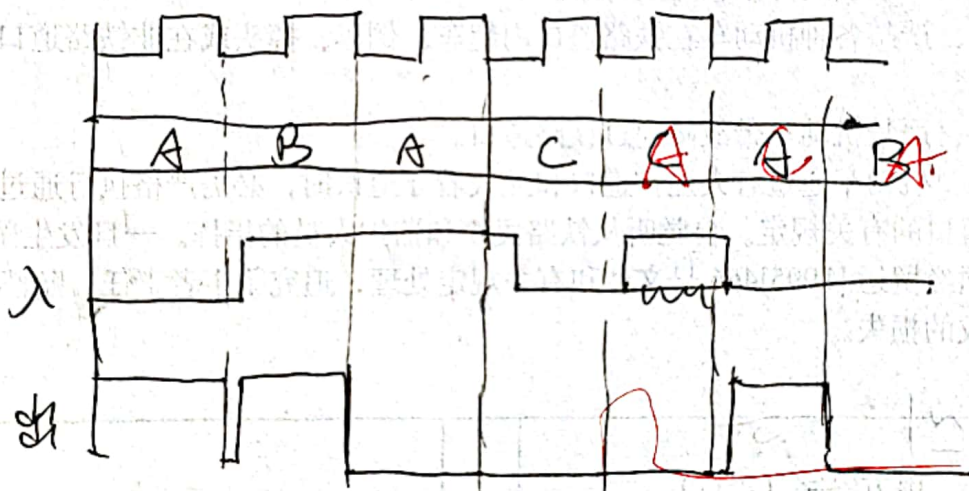

(1) $F_1 = Y_0 + Y_1 + Y_2 + Y_4 = \bar{Y}_0 \bar{Y}_1 \bar{Y}_2 \bar{Y}_4$

$= \prod M(0, 1, 2, 4) = \sum m(3, 5, 6, 7)$

$F_0 = Y_0 + Y_3 + Y_4 + Y_6 = \bar{Y}_0 \bar{Y}_3 \bar{Y}_4 \bar{Y}_6 = \prod M(0, 3, 5, 6)$

$= \sum m(1, 2, 4, 7)$

(2)

F_1	D_2	D_1	D_0
D_2	00	01	11
0	0	0	1
1	0	1	1

$F_1 = D_2 D_0 + D_2 D_1 + D_1 D_0$

F_0	D_2	D_1	D_0
D_2	00	01	11
0	0	1	0
1	1	0	0

$F_0 = D_2 \bar{D}_1 \bar{D}_0 + \bar{D}_2 \bar{D}_1 D_0 + D_2 D_1 D_0 + \bar{D}_2 D_1 \bar{D}_0$

(3)

D_2	D_1	D_0	F_1	F_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(4)

该电路功能

求 $D_2 + D_1 + D_0$

加法器

 F_0 是结果 F_1 是进位 F_1 是进位 $D_2 + D_1 + D_0$ 的结果

(11)

(2)


	P	C	B	A	F_1
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	0

(1)

$$F_1 = \prod M(0, 1, 3, 4, 6, 7, 9, 10, 12, 13, 15)$$

$$\begin{aligned}
 F_1 &= \bar{D}\bar{C}B\bar{A} + \bar{D}\bar{C}BA + D\bar{C}\bar{B}\bar{A} + D\bar{C}BA \\
 &\quad + DCB\bar{A} \\
 &= \bar{B}\bar{A}(\bar{D}\bar{C} + DC) + \bar{B}A(D\bar{C}) + \bar{B}A(\bar{D}C) + BA(D\bar{C}) \\
 &= m_0(\bar{D}\bar{C}) + m_1(\bar{D}\bar{C}) + m_2(D\bar{C}) + m_3(D\bar{C})
 \end{aligned}$$

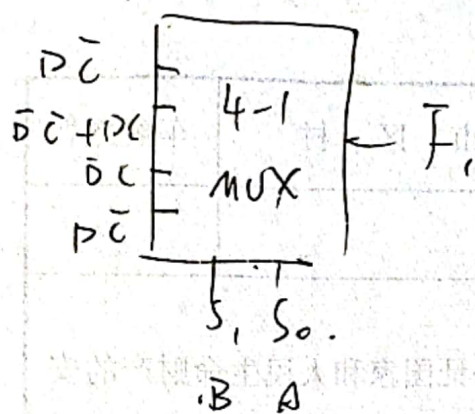故 $f_0 = D\bar{C}$ $f_1 = \bar{D}C$ $f_2 = \bar{D}\bar{C} + DC$ $f_3 = D\bar{C}$




7. (1) $P=T=1$, $A=B=1$ $C=D=0$.

$G=1$, $L_0 = \overline{Q_C Q_D} = \bar{Q}_C + \bar{Q}_D$

(2)

$M=10$ 10进制

(3)

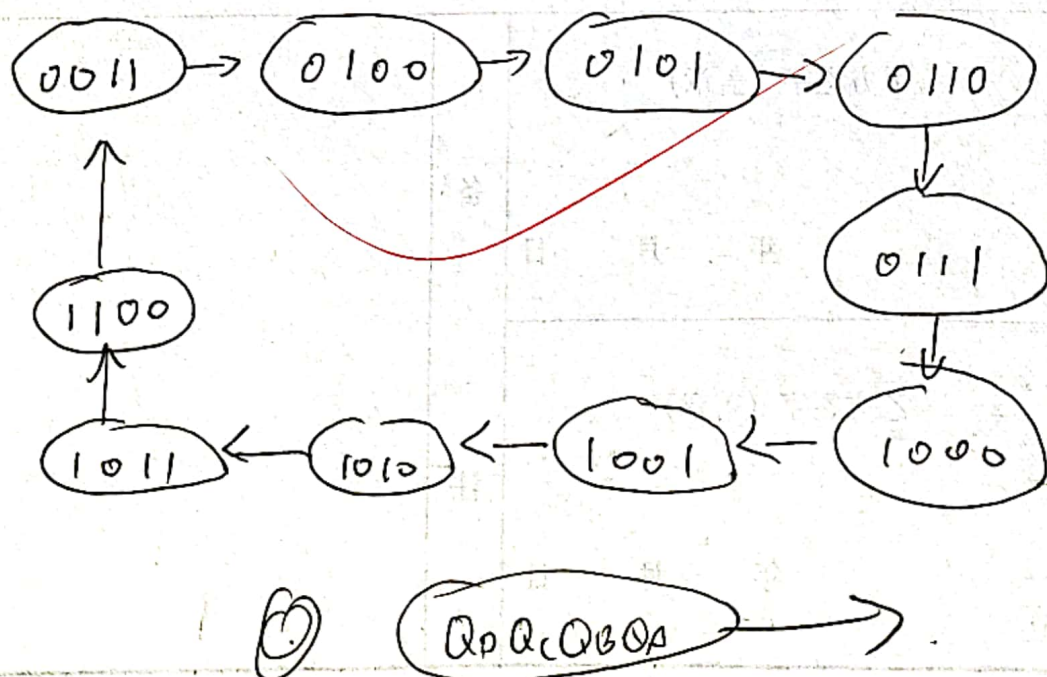

六、 $M=6$, 三个触发器 D_2, D_1, D_0

(1)

n			$n+1$		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	X	X	X
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	X	X	X
1	1	0	1	0	0
1	1	1	1	1	0

(2)

Q_2^{n+1}	$Q_2^n Q_1^n Q_0^n$			
	00	01	11	10
0	001	011	111	XXX
1	000	XXX	110	100

(3)

Q_2^{n+1}	$Q_2^n Q_1^n Q_0^n$			
	00	01	11	10
0	0	0	1	X
1	0	X	1	1

Q_1^{n+1}	$Q_2^n Q_1^n Q_0^n$			
	00	01	11	10
0	0	1	1	X
1	0	X	1	0

Q_0^{n+1}	$Q_2^n Q_1^n Q_0^n$			
	00	01	11	10
0	1	1	1	X
1	0	X	0	0

$010 \rightarrow 1010$

$101 \rightarrow 010$

不%自%动。

把 Q_2 010 改成 0

Q_2^{n+1}

	00	01	11	10
0	0	0	1	0
1	0	0	1	1

Q_1^{n+1}

	00	01	11	10
0	0	1	1	0
1	0	1	1	0

Q_0^{n+1}

	00	01	11	10
0	1	1	1	1
1	0	0	0	0

010 \rightarrow 001 \checkmark
 101 \rightarrow 010 \checkmark

(4) $Q_2^{n+1} = Q_2 Q_1 + Q_1 Q_0$

$Q_1^{n+1} = Q_0$

$Q_0^{n+1} = \overline{Q_2}$

(5) Q_2^{n+1}

	00	010	11	10
0	0	0	1	0
1	0	0	1	1

$J_2 = Q_1 Q_0$

$\overline{K}_2 = Q_1 \rightarrow K_2 = \overline{Q_1}$

Q_1^{n+1}

	00	01	11	10
0	0	1	1	0
1	0	1	1	0

$J_1 = Q_0$


$\overline{K}_1 = Q_0 \rightarrow K_1 = \overline{Q_0}$

Q_0^{n+1}

	00	01	11	10
0	1	1	1	1
1	0	0	0	0

$J_0 = \overline{Q_2}$

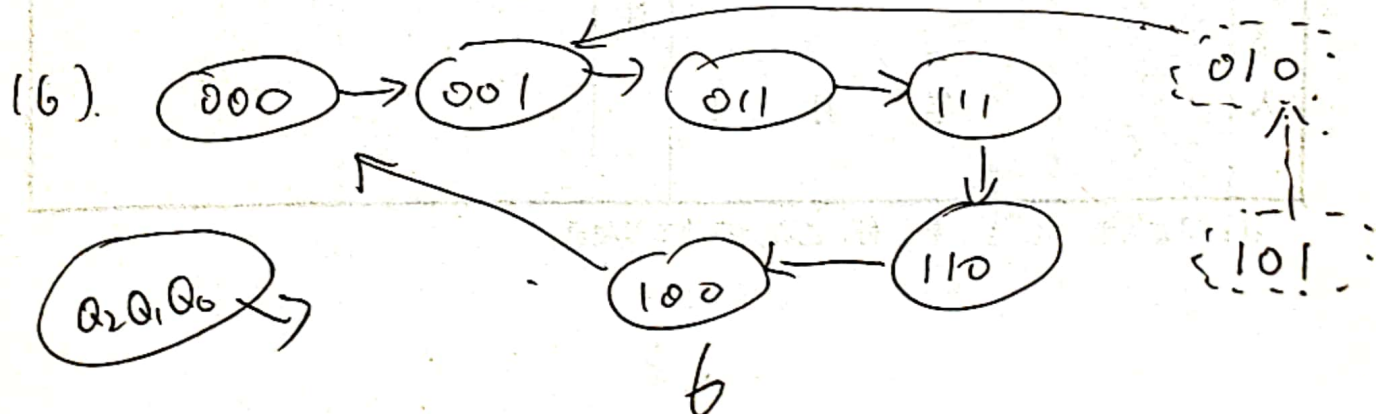$\overline{K}_0 = \overline{Q_2} \rightarrow K_0 = Q_2$



最终答案:


(1)

	n				$n+1$			
	Q_2	Q_1	Q_0		Q_2	Q_1	Q_0	
0	0	0	0		0	0	1	1
1	0	0	1		0	1	1	3
2	0	1	0		0	0	1	1
3	0	1	1		1	1	1	7
4	1	0	0		0	0	0	0
5	1	0	1		0	1	0	2
6	1	1	0		1	0	0	4
7	1	1	1		1	1	0	6

(2)

Q_2	$Q_1 Q_0 00$	01	11	10
0	001	011	111	001
1	000	010	110	100


(3) 无效状态

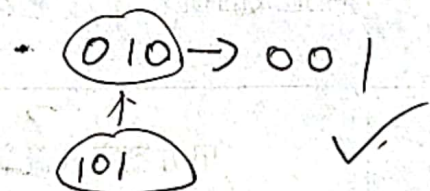

(3) 可以自启动.

$J_2 = Q_1 Q_0$ $J_1 = Q_0$ $J_0 = \bar{Q}_2$
 $K_2 = \bar{Q}_1$ $K_1 = \bar{Q}_0$ $K_0 = Q_2$

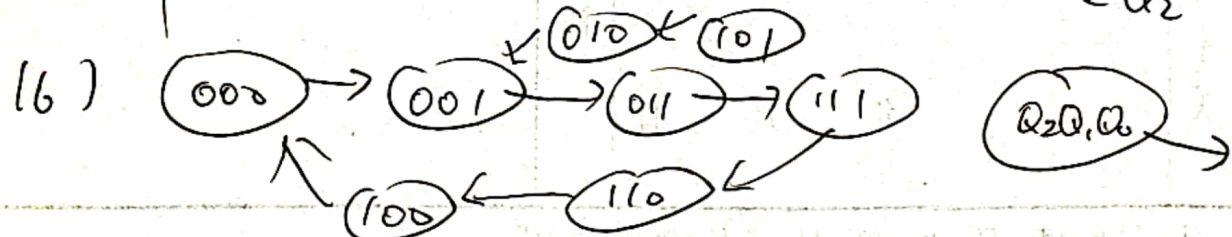(14) $Q_2^{n+1} = Q_2 Q_1 + Q_1 Q_0$ $Q_1^{n+1} = Q_0$ $Q_0^{n+1} = \bar{Q}_2$



(7) Q_2, Q_1, Q_0 均可, 经输出, 均分 6 份