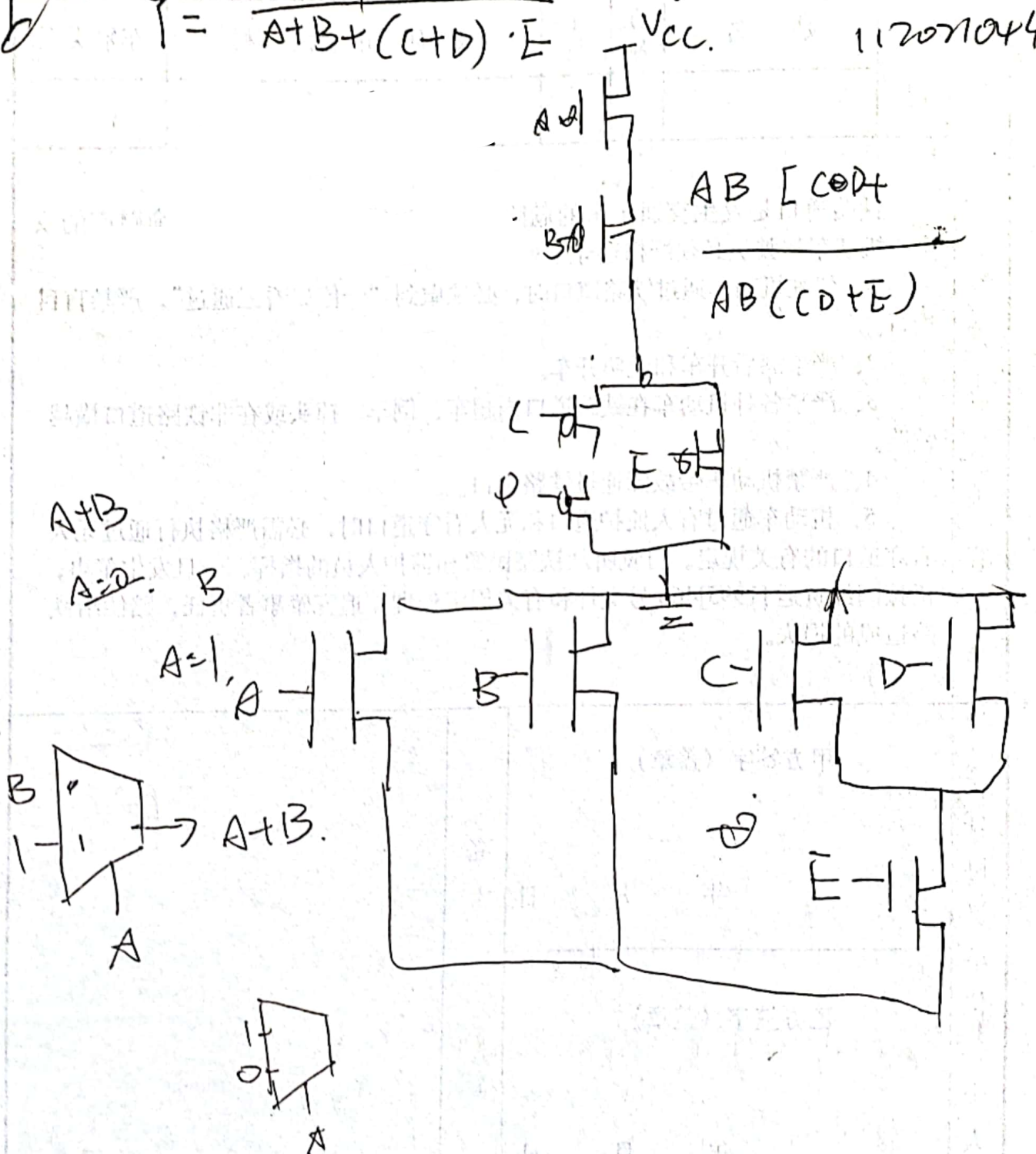


2022年数电, 可考, 王瑞

b  $Y = \overline{A+B+(C+D) \cdot E}$   $V_{CC}$  1120710446




0000	0000	0
0001	0000	1
0010	0000	2
0011	0000	3
0100	0000	4
0101	0001	5
0110	0010	6
0111	0011	7
1000	0000	8
1001	0010	9
1010	0100	10
1011	0110	11
1100	0000	12
1101	0011	13
1110	0110	14
1111	1001	15

$$Y_3 = \sum m(15)$$

$$Y_2 = \sum m(10, 11, 14)$$

$$Y_1 = \sum m(6, 7, 9, 11, 13, 14)$$

$$Y_0 = \sum m(5, 7, 13, 15)$$

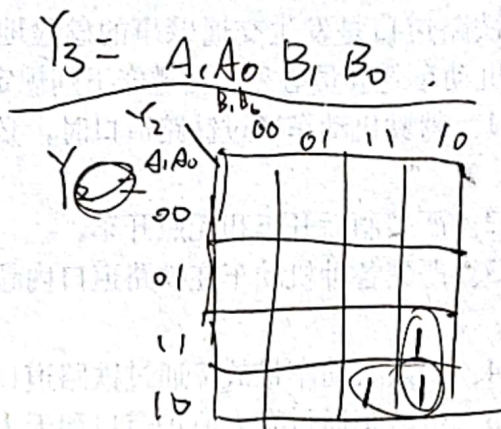



$$Y_2 = \overline{A_1} \overline{A_0} B_1 + A_1 B_1 \overline{B_0}$$

$$= A_1 B_1 (\overline{A_0} + \overline{B_0})$$


$$Y_1 = \overline{A_1} A_0 B_1 + A_0 B_1 \overline{B_0}$$

$$+ A_1 A_0 B_0 + A_1 B_1 B_0$$

$$Y_0 = A_0 B_0$$

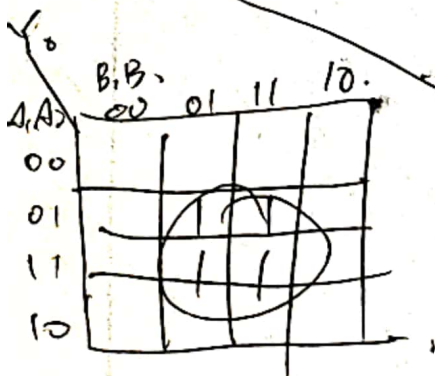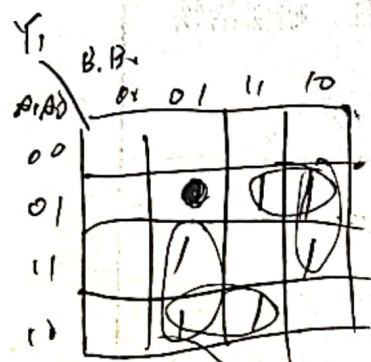
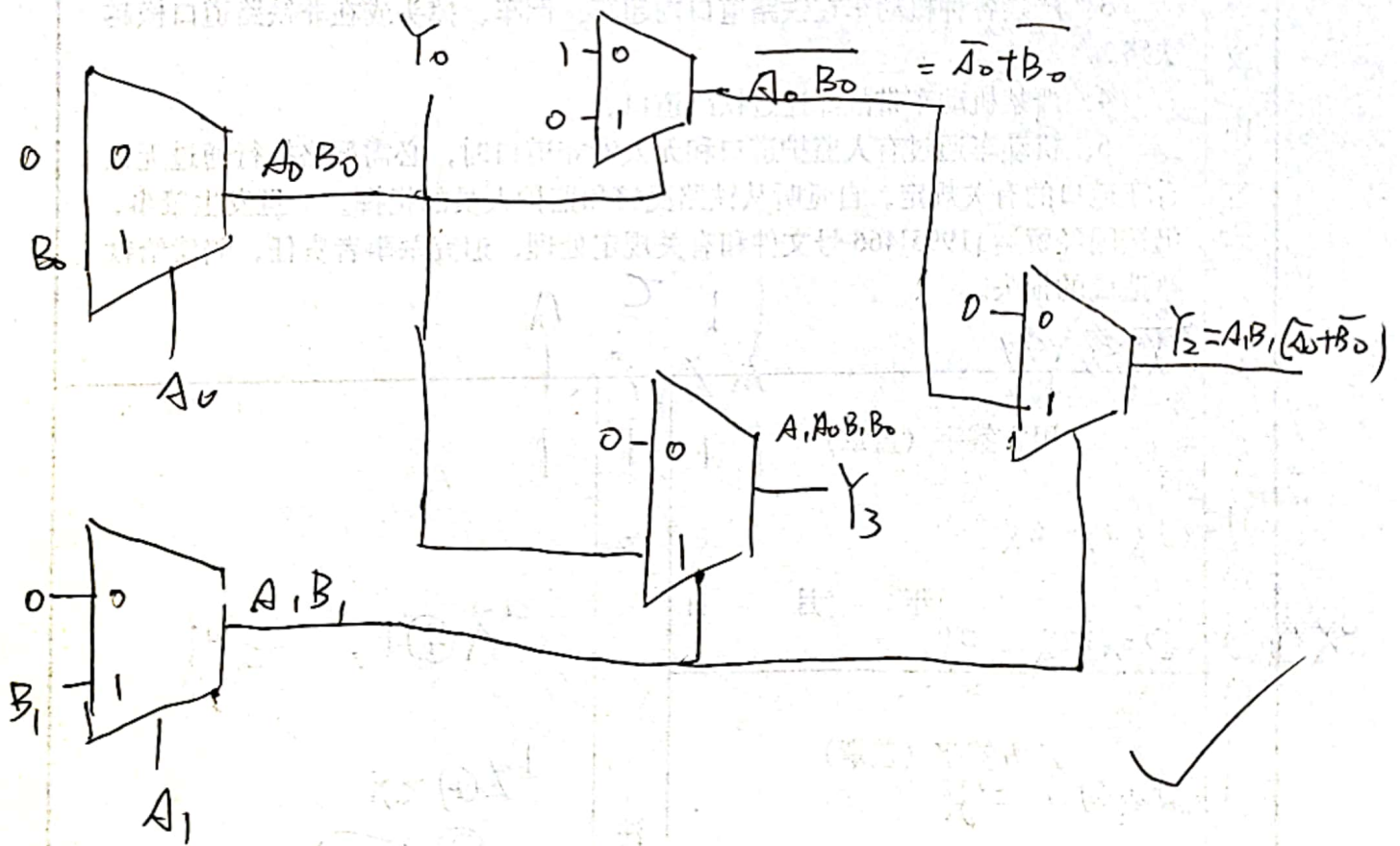
$$\overline{A_0 + B_0} = \overline{A_0 B_0}$$



2



3.

$$(1) Y_3 = X_3$$

$$Y_2 = X_2 \oplus X_3 = \bar{X}_2 X_3 + X_2 \bar{X}_3$$

$$Y_1 = \overline{X_2 \oplus Y_2} \oplus X_1$$

$$= (X_2 + Y_2) \oplus X_1$$

$$= [X_2 + \bar{X}_2 (X_2 \oplus X_3)] \oplus X_1$$

$$Y_0 = \overline{X_1 \oplus Y_1} \oplus X_0$$

$$= (X_1 + Y_1) \oplus X_0$$


$$= [X_1 + \bar{X}_1 (X_2 + \bar{X}_2 (X_2 \oplus X_3))] \oplus X_0$$

(2)  $m=1$  时, 将  $X_3 X_2 X_1 X_0$  转换为格雷码.

即  $X_3 X_2 X_1 X_0$  的格雷码为  $Y_3 Y_2 Y_1 Y_0$

$m=0$  时, 将  $X_3 X_2 X_1 X_0$  转换为二进制的码, 即解格雷码, 即西格雷码  $X_3 X_2 X_1 X_0$  的二进制码为  $Y_3 Y_2 Y_1 Y_0$

4.

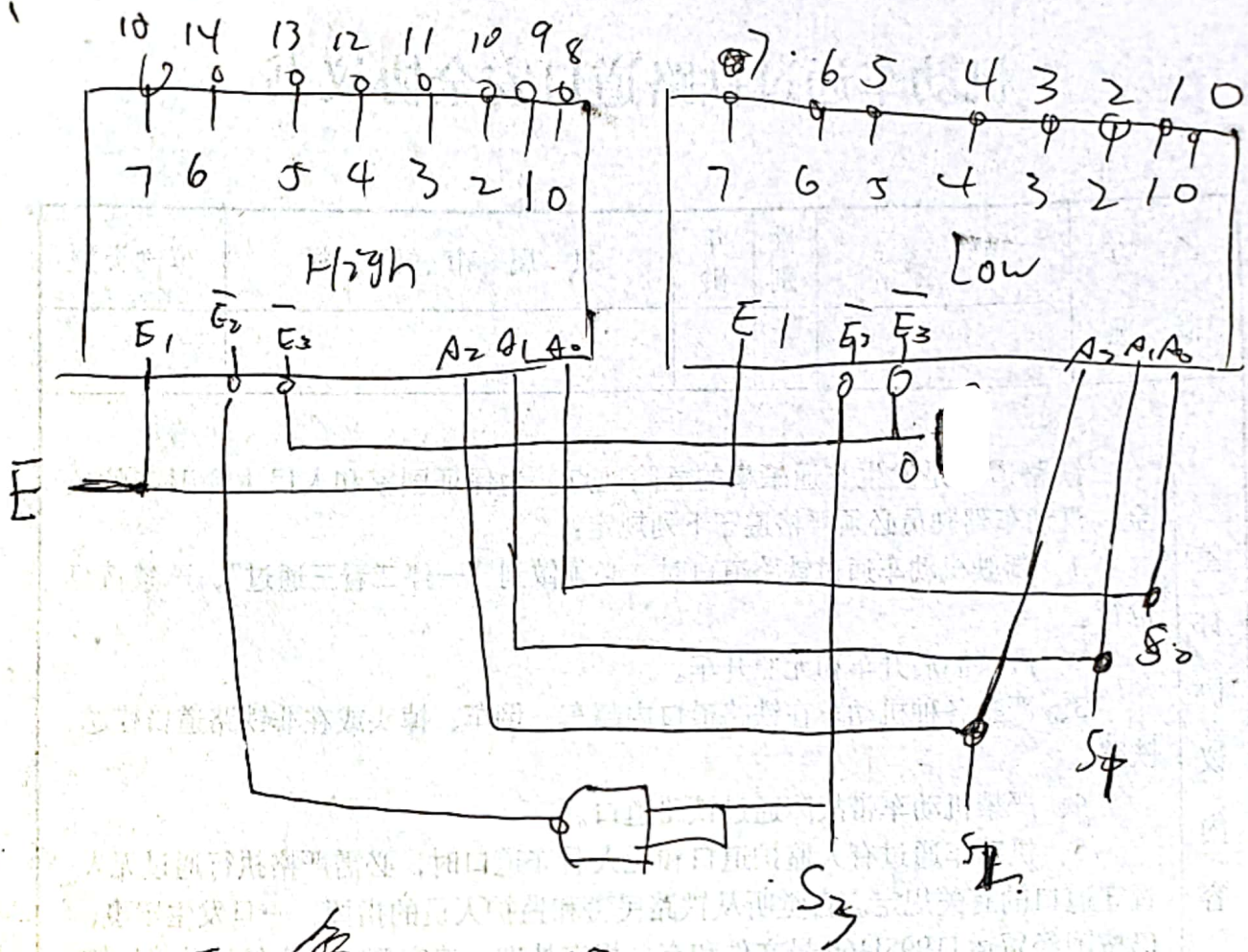

5.

	$\bar{A}$	$A$	$\bar{B}$	$B$	$AB$	$\bar{A}\bar{B}$
$\bar{A}\bar{B}$	1	0	1	0	0	1
$\bar{A}B$	0	1	1	0	1	0
$A\bar{B}$	0	0	1	1	0	1
$AB$	0	1	0	1	1	0

Output:  $S_3, S_2, S_1, S_0$

$$F = \sum m(0, 3, 5, 7)$$

$$F = \sum m(0, 3, 5, 7, 8, 9, 10, 11, 15)$$

5




	$y_1 y_0$	00	01	11	10
$x_1 x_0$	00	1	0	1	0
	01	0	1	1	0
	11	0	0	1	0
	10	1	1	1	1

$$F = (\bar{x}_0 + \bar{y}_0) (\bar{x}_1 + \bar{x}_0 + y_1) (\bar{x}_0 + y_1 + \bar{y}_0) (x_1 + x_0 + y_1 + \bar{y}_0)$$

$$F = \bar{x}_0 + \bar{y}_0 + \bar{y}_1 + \bar{x}_0 + y_1 + x_1 + \bar{y}_1 + \bar{y}_0 + x_1 + x_0 + y_1 + \bar{y}_0$$


6

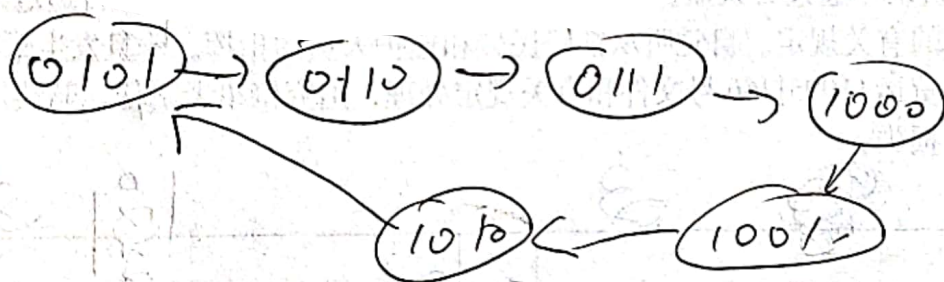

$M=6$


(1) 1010

5, 6, 7, 8, 9, 10,  $M=6$

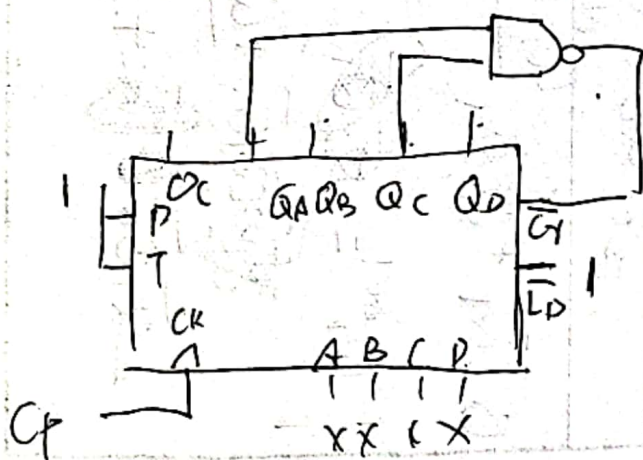


0-5

0 1 2 3 4 5 ✓

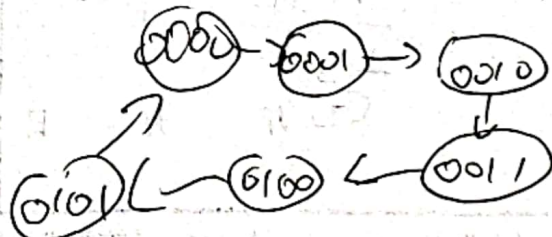

6

(2)

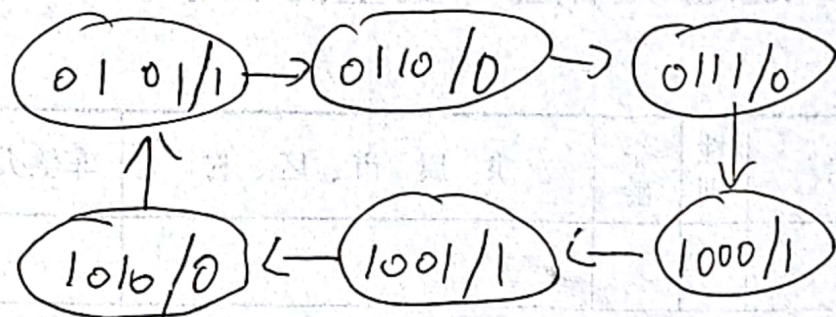

$Q_2 Q_1 Q_0 / Z$

(3) 100110

(4) 3 ↑

7. 1)  $Q_2^{n+1}$   $Q_1 Q_0$

2)  $Q_2$

$Q_2$	$Q_1 Q_0$	00	01	11	10
0	0	1	0	0	0
1	0	1	1	0	1
	1				
	0				

$Q_1^{n+1}$   $Q_1 Q_0$

$Q_2$

$Q_2$	$Q_1 Q_0$	00	01	11	10
0	0	0	0	0	0
1	0	1	1	1	1
	1				
	0				

$Q_0^{n+1}$   $Q_1 Q_0$

$Q_2$

$Q_2$	$Q_1 Q_0$	00	01	11	10
0	0	1	0	1	1
1	0	1	0	0	1
	1				
	0				

$$J_2 = \bar{Q}_1 \bar{Q}_0$$

$$K_2 = \bar{Q}_1 + \bar{Q}_0$$

$$\Rightarrow K_2 = Q_1 Q_0$$

$$J_1 = Q_2$$

$$\bar{K}_1 = Q_2 \Rightarrow K_1 = \bar{Q}_2$$


$$J_0 = 1$$

$$\bar{K}_0 = \bar{Q}_2 Q_1 \Rightarrow K_0 = Q_2 + \bar{Q}_1$$


7



3)

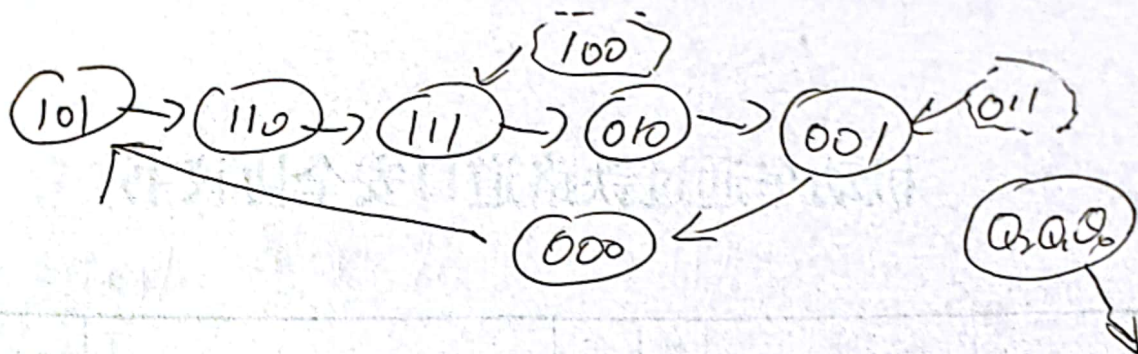

14)

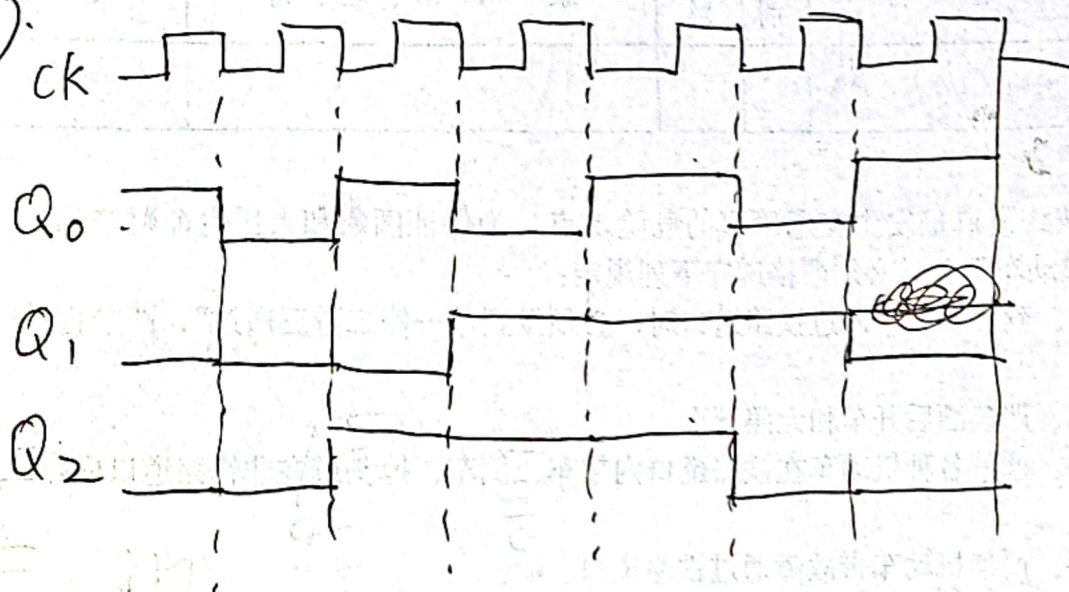

001 000 101 110 111 010 001

10)  $Q_0$  = 分步,  $Q_1, Q_2$  = 六分步

8. 思路: 每次有满4个时钟周期, 再反向输出

可以用移位寄存器实现

